



Lesson Sequence



1. Understand electrical appliances and safety



2. Learn about electrical compounds in a series circuit



3. Investigate electrical circuits



4. Explore conductors and insulators



5. Learn about electrical switches



6. Investigate how electrical components can change within a circuit


Key Facts

1. A circuit contains a battery (cell), wires and a component that requires electricity to work (bulb, motor or buzzer).
2. Electrical current flows through the wires from the battery (cell) to the bulb, motor or buzzer.
3. A switch can break or reconnect a circuit.
4. A switch controls the flow of the electrical current around the circuit. When the switch is off, the current cannot flow. This is not the same as an incomplete circuit.

Conductors and Insulators

- Materials that allow electricity to pass through to create a complete circuit are called electrical conductors.
- Materials that do not allow electricity to pass through and do not complete a circuit are called electrical insulators.

conductors	
steel	copper
insulators	
wood	plastic

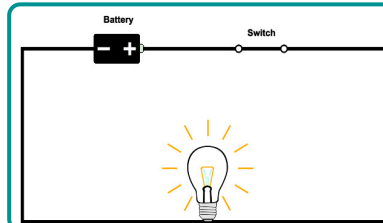


Simple Circuit

A **complete** circuit is a **loop** that allows electrical current to flow through wires.



Simple Electrical Circuit

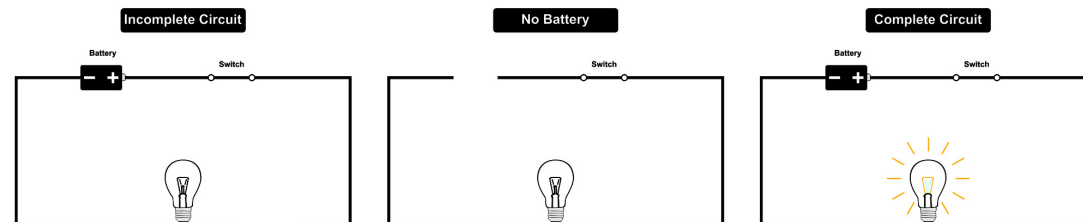These are complete circuits - they have a battery (cell) and a component (bulb). The wires are placed in the right places of the battery for the circuit to work.



These circuits will not work as they are incomplete.

Electrical Components

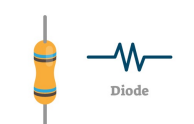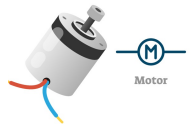



Another name for a battery is:	before	after
circuit		
buzzer		
light		
cell		

How will you know if a material conducts electricity?	before	after
Electricity will flow freely, and the circuit will work		
Electricity will not flow, and the circuit will not work		
The battery will not work		

Which of these need electricity to work?	before	after
torch		
mobile phone		
games console		
car		

When more batteries are added to a complete circuit...	before	after
the light bulb does not go on		
the light bulb becomes brighter		
the circuit does not work		
the switch goes off		

A circuit will not work if....(tick three):	before	after
there is no battery		
the switch is off		
there is a break in the circuit		
there is no switch		

Objects that are made from materials that do not allow electricity to pass through are called:	before	after
conductors		
insulators		
batteries		

Why is it dangerous to use an electrical appliance near water?

	Before	After

Draw the electrical symbol for the components below.

		Before	After
